

2020-09-16/MS

## Signal Processing, #3

### Topics:

- Frequency transformations: LP  $\rightarrow$  HP, LP  $\rightarrow$  BP and LP  $\rightarrow$  BS
- Sensitivity analysis

### Literature:

Kendal Su: "Analog Filters", Kluwer Academic Publishers, 2<sup>nd</sup> ed. 2002, ISBN 1-4020-7033-0

The book is available in electronic form at <http://www.en.aub.aau.dk>.

Topic	Pages ({*} $\Leftrightarrow$ supplementary lit.)
Inverse Chebyshev characteristic	37-38
Bessel/Thomson characteristic	{66-71}
Frequency transformations	77-88
Sensitivity analysis	171-184

Supplementary: Lecture presentation "slides"

### Exercises:

#### 3.1

A Chebyshev filter must pass frequencies above 1 kHz (not rad/s) with max. 0.5 dB attenuation and must attenuate frequencies below 100 Hz with at least 60 dB.


- Make a rough sketch of the filter requirements.
- Find the necessary filter order,  $n$ , using the HP $\leftrightarrow$ LP frequency mapping, and the " $n =$ " equation from the slides from lecture 2
- Find (analytically) the actual attenuation at 100 Hz.
- Check the result in c. by making a plot in Matlab.
- A normalized 3<sup>rd</sup> order Chebyshev LP-filter with 0.5 dB ripple can be made using the circuit shown with:

$$L_1 = 1.3465 \text{ H}$$

$$C_2 = 1.3001 \text{ F}$$

$$L_3 = 0.7981 \text{ H}$$

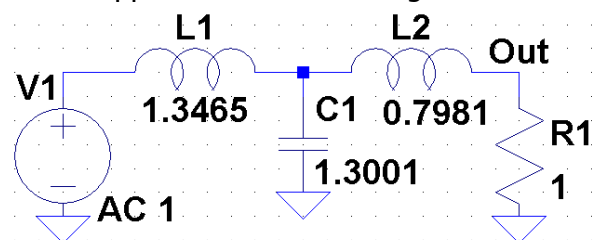Find the component values in a 1 kHz HP-filter.



#### 3.2

A BP-filter made from a 4<sup>th</sup> order LP-prototype has:

- Butterworth characteristic
  - Lower passband edge (-3 dB) = 10 kHz
  - Upper passband edge (-3 dB) = 15 kHz
- Find (analytically) the attenuation at 1 kHz and 20 kHz using the frequency transformation and  $|H(j\omega)|^2$  for the low-pass prototype.
  - Check the result in a. by making a plot in Matlab.

### 3.3

Use Matlab to plot the step response of 5<sup>th</sup> order low-pass filters:

- Butterworth ( $\omega_{-3dB} = 1$  rad/s)
  - Elliptic with 1 dB passband ripple and 40 dB stopband attenuation. It must be re-normalized to have a 3 dB cut-off radian frequency of 1 rad/s to make a fair comparison.
- a. Make a Bode-plot to check the re-normalization.
  - b. Plot step-responses

### 3.4

A high-pass filter section has the transfer function:

$$H(s) = - \frac{\frac{C_1}{C_2} s^2}{s^2 + \frac{C_1 + C_2 + C_3}{R_2 C_2 C_3} s + \frac{1}{R_1 R_2 C_2 C_3}}$$

The capacitor values are:

- $C_1 = 10$  nF,  $C_2 = 15$  nF and  $C_3 = 15$  nF

- a. Find an expression for Q as a function of the component values.
- b. Find the sensitivity of Q with respect to  $C_1$ ,  $S_{C_1}^Q$

**Results:****3.1**

- a.
- b. *3*
- c. *62.8 dB*
- d.
- e. *118  $\mu F$ , 122  $\mu H$ , 199  $\mu F$*

**3.2**

- a. *118 dB, 31.8 dB*
- b.

**3.3**

- a.
- b.

**3.4**

- c.
- d. *-0.25*