

EIT5/ITC5 Signal Processing, 4

Topics:

- OpAmps applied in active RC-filters
- Various designs of 2nd order Sallen-Key LP-filters
- MFB-filters
- HP, BP and BS filters
- In brief: Section allocation, effect of limited operational amplifier gain

Literature:

Kendal Su: "Analog Filters", Kluwer Academic Publishers, 2nd ed. 2002, ISBN 1-4020-7033-0

The book is available in electronic form at <http://www.en.aub.aau.dk>.

| Topic | Pages ({*} ⇔ supplementary lit.) |
|--------------------------------|-------------------------------------|
| Operational amplifier circuits | 187-189, {190-196}, 206-208 |
| Biquad circuits | 204-206, 217-238 |
| Higher order filters | 253-260, 263-264 |

Supplementary: Lecture presentation "slides"


Preparation: I assume that basic operational amplifier circuits are well known to you. If you are in doubt, please read page 190-196.

Exercises:

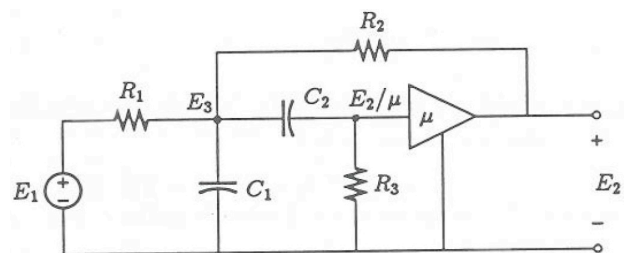4.1

The filter in Kendall Su: "Analog filters" Figure 8.4 has the transfer function given in (8.22). Component values are chosen as: $C_1 = C_2 = C$, $R_1 = R_2 = R$ and $R_3 = 2R$. In this case the transfer function can be reduced to:

$$H(s) = \frac{\frac{\mu}{CR}s}{s^2 + \frac{3-\mu}{CR}s + \frac{1}{(CR)^2}}$$



- Find expressions for ω_0 and Q
- Find an expression for S_μ^Q and its value for $Q = 5$
- Find a simple expression for $H(j\omega_0)$ and for $S_\mu^{H(j\omega_0)}$ and their values for $Q = 5$

4.2

A 2nd order Butterworth normalized low-pass prototype filter is transformed to a BP-filter (4 poles) having:

- Lower passband edge (-3 dB) = 10 kHz
- Upper passband edge (-3 dB) = 15 kHz

The filter is made using 2 biquad filter sections of the type analyzed in exercise 4.1

a. Find the pole locations of the BP-filter. Hint: Use Matlab:

```
OrderLPP = 2;
Om = [10 15]*pi*2e3;
[Numpoly DenomPoly] = butter(OrderLPP,Om,'s'); % Bandpass since Om
is a vector
Poles = roots(DenomPoly)
```


b. Find ω_0 and Q for each of the two sections. Hint:

```
omeg_0_biquad = abs(Poles)
Q_biquad = % some function of Poles
```

c. Using $C = 1$ nF, find the resistor values and μ in each section.

| Section | $\omega_0 [10^4 \text{ rad/s}]$ | Q | $R = R_1 = R_2$ | $R_3 = 2R$ | μ |
|---------|---------------------------------|-----|-----------------|-----------------|-------|
| 1 | 8.90 | 3.5 | 11.2 k Ω | 22.5 k Ω | 2.71 |
| 2 | | | k Ω | k Ω | |

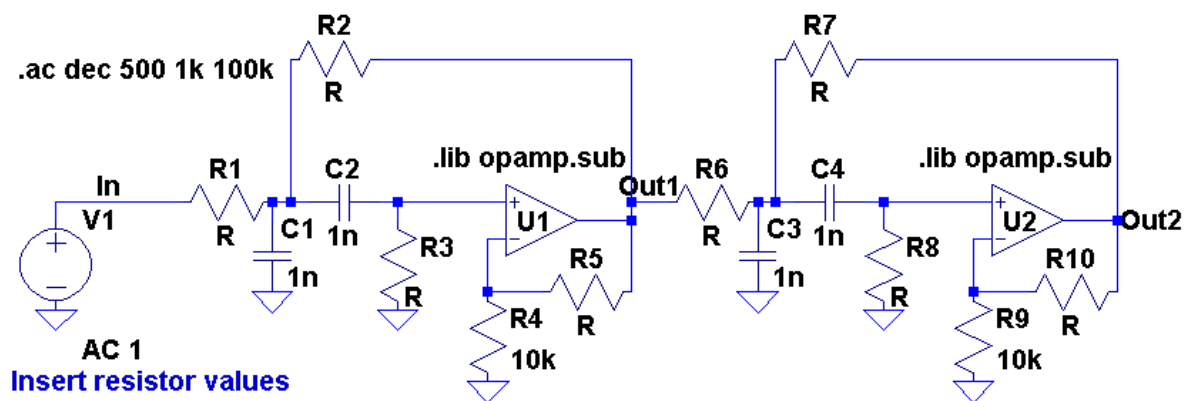
d. Option: Make a Spice-simulation to check the results (Hint: LT-Spice example):



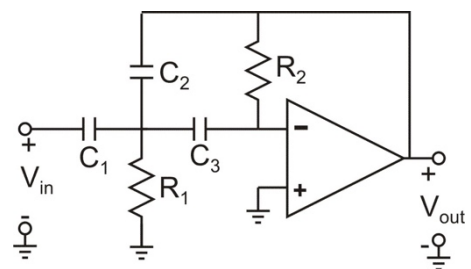4.3

The 2nd order MFB high-pass section shown has the transfer function:

$$H(s) = -\frac{\frac{C_1}{C_2} s^2}{s^2 + \frac{C_1 + C_2 + C_3}{R_2 C_2 C_3} s + \frac{1}{R_1 R_2 C_2 C_3}}$$



The capacitor values are chosen as:

- $C_1 = C_2 = 10$ nF
- $C_3 = 2C_1 = 2C_2 = 20$ nF

and it is required that:

- $\omega_0 = 2\pi \cdot 10^4$ rad/s
- $Q = 5$

a. Find the values of R_1 and R_2

b. Find the filter gain, $|H(j\omega_0)|_{\text{dB}}$, at ω_0 .

c. Find the filter gain, $|H(j\omega)|_{\text{dB}}$, for $\omega \rightarrow \infty$

4.4

A 2nd order Butterworth normalized low-pass prototype filter is transformed to a BP-filter (4 poles) having (same data as in ex. 4.2):

- Lower passband edge (-3 dB) = 10 kHz
- Upper passband edge (-3 dB) = 15 kHz

The filter is made using 2 biquad filter sections:

- An MFB low-pass section, for the poles with the largest ω_0 , with $R_1 = R_2 = R_3 = R = 2 \text{ k}\Omega$.
- An SK high-pass section, for the poles with the smallest ω_0 , with $C_1 = C_2 = C = 10 \text{ nF}$ and $\mu = 1$.

- Find the pole locations of the BP-filter using Matlab
- Find ω_0 and Q for each of the two sections from the pole locations.

| Section | $\omega_0 [10^4 \text{ rad/s}]$ | Q |
|----------|---------------------------------|------------|
| 1 MFB-LP | <i>8.90</i> | <i>3.5</i> |
| 2 SK-HP | | |

- Find the component values of the MFB-LP section
- Find the component values of the SK-HP section.
- Option: Make a Spice-simulation to check the results (Exerc5_2template.asc)

Results:**4.1**

-
- 14*
- 14, 15*

4.2

- 12710±j88077 and -9504±j65862*
- 88989/66545 3.5/3.5*

4.3

- 79.6 Ω , 15.9 k Ω*
- 14 dB*
- 0 dB*

4.4

- 12710±j88077, -9504±j65862*
-
- 59.0 nF, 535 pF*
- 215 Ω , 10.5 k Ω*
-