

EIT/ITC5 Signal Processing, 4

Suggested solutions to exercises:

4.1

The filter in Kendall Su: "Analog filters" Figure 8.4 has the transfer function given in (8.22). Component values are chosen as: $C_1 = C_2 = C$, $R_1 = R_2 = R$ and $R_3 = 2R$. In this case the transfer function can be reduced to:

$$H(s) = \frac{\frac{\mu}{CR} s}{s^2 + \frac{3-\mu}{CR} s + \frac{1}{(CR)^2}}$$

- a. Find expressions for ω_0 and Q

$$\omega_0 = \frac{1}{CR} \quad \frac{3-\mu}{CR} = \frac{\omega_0}{Q} = \frac{1}{CRQ} \Rightarrow \underline{\underline{Q = \frac{1}{3-\mu}}}$$

- b. Find an expression for S_μ^Q and its value for $Q = 5$

$$S_\mu^Q = -S_\mu^{(3-\mu)} = \frac{-\mu}{3-\mu} \cdot \frac{\partial(3-\mu)}{\partial\mu} = \frac{\mu}{3-\mu}$$

$$Q = \frac{1}{3-\mu} \Leftrightarrow 3Q - \mu Q = 1 \Leftrightarrow \mu = 3 - \frac{1}{Q}$$

$$\underline{\underline{S_\mu^Q = Q \left(3 - \frac{1}{Q} \right) = 3Q - 1}}$$

$$Q = 5 \Rightarrow \underline{\underline{S_\mu^Q = 14}}$$

This is similar to the value found in the slides

- c. Find a simple expression for $H(j\omega_0)$ and for $S_\mu^{H(j\omega_0)}$ and their values for $Q = 5$

$$\underline{\underline{H(j\omega_0) = H(s)|_{s=j\omega_0}}} = \frac{\frac{\mu}{CR} s}{s^2 + \frac{3-\mu}{CR} s + \frac{1}{(CR)^2}} \bigg|_{s=j\omega_0} = \frac{\frac{\mu}{CR}}{\frac{3-\mu}{CR}} = \frac{\mu}{3-\mu} = \underline{\underline{\mu Q}}$$

$$\underline{\underline{S_\mu^{H(j\omega_0)}}} = \frac{\frac{\mu}{3-\mu}}{\frac{\mu}{3-\mu}} \cdot \frac{\partial \frac{\mu}{3-\mu}}{\partial\mu} = (3-\mu) \left(\frac{1}{3-\mu} + \frac{\mu}{(3-\mu)^2} \right) = 1 + \frac{\mu}{3-\mu} = \frac{3}{3-\mu} = \underline{\underline{3Q}}$$

$$(an easier way: S_\mu^{\mu Q} = S_\mu^\mu + S_\mu^Q = 1 + S_\mu^Q = 1 + (3Q - 1) = 3Q)$$

$$Q = 5 \Rightarrow \mu = 3 - \frac{1}{Q} = 2.8 \Rightarrow \underline{\underline{H(j\omega_0) = 14}} \quad \underline{\underline{S_\mu^{H(j\omega_0)} = 15}}$$

4.2

A 2nd order Butterworth normalized low-pass prototype filter is transformed to a BP-filter (4 poles) having:

- Lower passband edge (-3 dB) = 10 kHz
- Upper passband edge (-3 dB) = 15 kHz

The filter is made using 2 biquad filter sections of the type analyzed in exercise 4.1

- a. Find the pole locations of the BP-filter. Hint: Use Matlab:

```
OrderLPP = 2;
Om = [10 15]*pi*2e3;
[Numpoly DenomPoly] = butter(OrderLPP,Om,'s'); % Bandpass since Om
is a vector
Poles = roots(DenomPoly)
Poles =
    1.0e+004 *
    -1.2710 + 8.8077i
    -1.2710 - 8.8077i
    -0.9504 + 6.5862i
    -0.9504 - 6.5862i
```

- b. Find ω_0 and Q for each of the two sections. Hint:

```
omeg_0_biquad = abs(Poles)
Q_biquad = -2\abs(Poles)./real(Poles) % some function of Poles
omeg_0_biquad =
    1.0e+004 *
    8.8989
    8.8989
    6.6545
    6.6545
Q_biquad =
    3.5007
    3.5007
    3.5007
    3.5007
```


- c. Using $C = 1$ nF, find the resistor values and μ in each section.


$$\mu = 3 - \frac{1}{Q} \quad R = \frac{1}{\omega_0 C}$$

Section	$\omega_0 [10^4 \text{ rad/s}]$	Q	$R = R_1 = R_2$	$R_3 = 2R$	μ
1	8.90	3.5	11.2 k Ω	22.5 k Ω	2.71
2	6.65	3.5	15.0 k Ω	30.1 k Ω	2.71

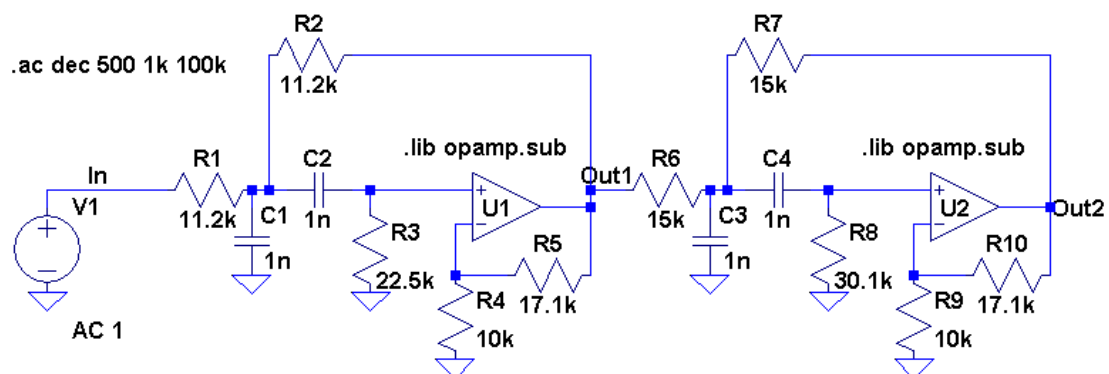- d. Optional Spice simulation:

Check: $20 \cdot \log_{10}(\mu Q) = 19.5 \text{ dB}$, 2 sections $< 39 \text{ dB}$ since the peaks are not coincident.




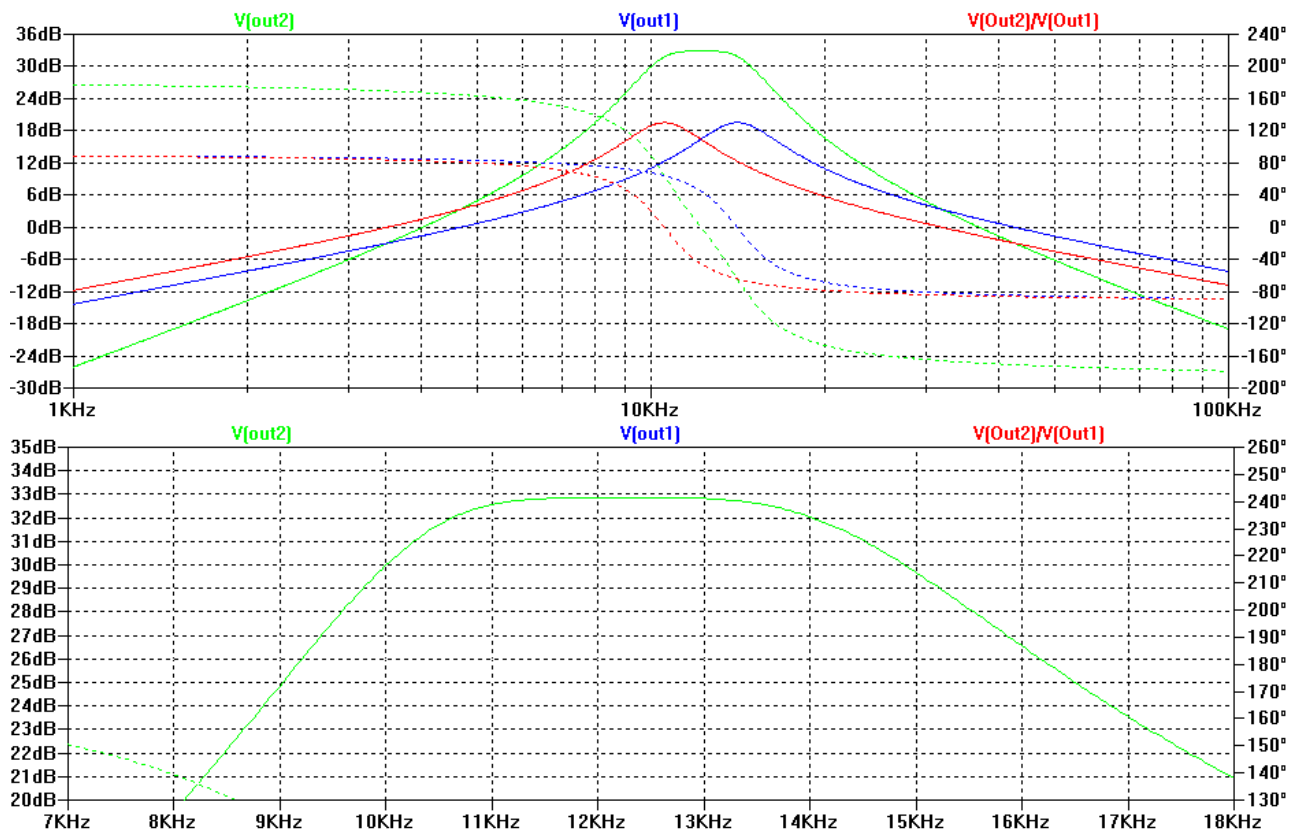

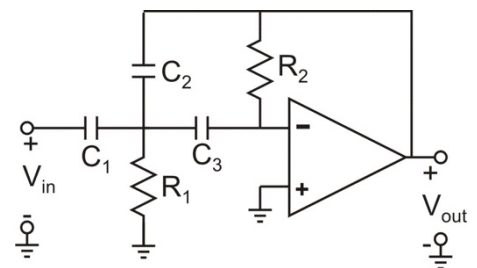4.3

The 2nd order MFB high-pass section shown has the transfer function:

$$H(s) = -\frac{\frac{C_1}{C_2} s^2}{s^2 + \frac{C_1 + C_2 + C_3}{R_2 C_2 C_3} s + \frac{1}{R_1 R_2 C_2 C_3}}$$



The capacitor values are chosen as:

- $C_1 = C_2 = 10 \text{ nF}$
- $C_3 = 2C_1 = 2C_2 = 20 \text{ nF}$

and it is required that:

- $\omega_0 = 2\pi \cdot 10^4 \text{ rad/s}$
- $Q = 5$

- Find the values of R_1 and R_2
- Find the filter gain, $|H(j\omega_0)|$, at ω_0 .
- Find the filter gain, $|H(j\omega)|$, for $\omega \rightarrow \infty$

Suggested solution:

- Comparing the transfer function with the standard second order function [K.S. (10.15) or mm.5.slide19/33) gives:

$$\frac{\omega_0}{Q} = \frac{C_1 + C_2 + C_3}{R_2 C_2 C_3} = \frac{2}{R_2 C_1} \Leftrightarrow Q = \frac{\omega_0}{2} R_2 C_1$$

$$\omega_0 = \sqrt{\frac{1}{R_1 R_2 C_2 C_3}} = \frac{1}{C_1 \sqrt{2 R_1 R_2}}$$

$$Q = \sqrt{\frac{R_2}{R_1}} \cdot \frac{1}{2\sqrt{2}} = 5 \Leftrightarrow \frac{R_2}{R_1} = (2\sqrt{2} \cdot 5)^2 = 200$$

$$\omega_0 = \frac{1}{\sqrt{400 \cdot C_1 R_1}} \Leftrightarrow$$

$$R_1 = \frac{1}{20 \omega_0 C_1} = \frac{1}{20 \cdot 2\pi \cdot 10^4 \cdot 10 \cdot 10^{-9}} = \underline{\underline{79.58 \Omega}}$$

$$\underline{\underline{R_2 = 200 R_1 = 15.92 \text{ k}\Omega}}$$


b. For $C_1 = C_2$ you get:

$$\underline{\underline{|H(j\omega_0)|}} = \left| -\frac{\frac{C_1}{C_2} s^2}{s^2 + \frac{C_1 + C_2 + C_3}{R_2 C_2 C_3} s + \frac{1}{R_1 R_2 C_2 C_3}} \right|_{s=j\omega_0} = \left| -\frac{s^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2} \right|_{s=j\omega_0} = \underline{\underline{Q = 5 \sim 14 \text{ dB}}}$$

c.

$$\lim_{\omega \rightarrow \infty} |H(j\omega)| = \frac{C_1}{C_2} = 1 \sim 0 \text{ dB}$$

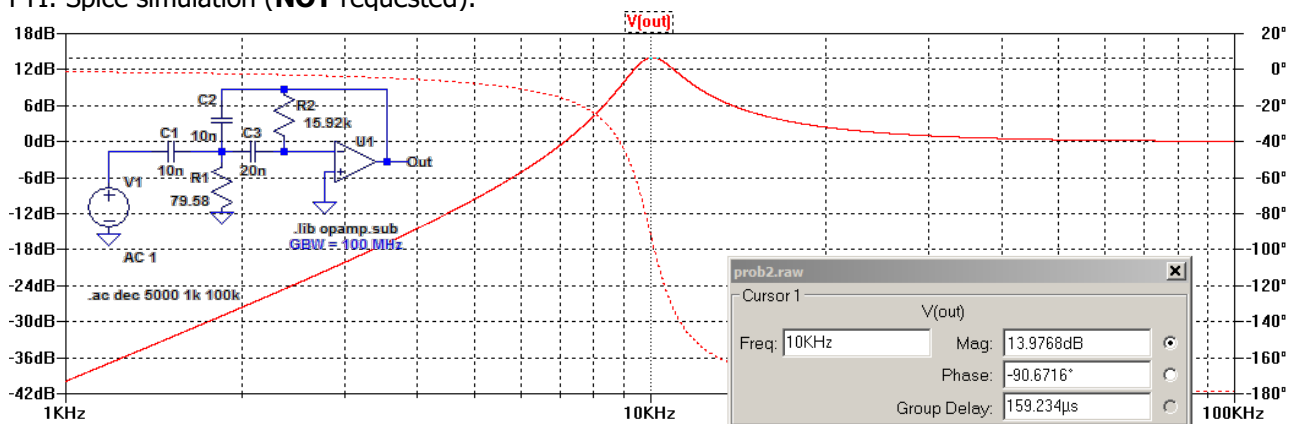FYI: Spice simulation (**NOT** requested):



4.4

A 2nd order Butterworth normalized low-pass prototype filter is transformed to a BP-filter (4 poles) having:

- Lower passband edge (-3 dB) = 10 kHz
- Upper passband edge (-3 dB) = 15 kHz

The filter is made using 2 biquad filter sections:

- An MFB low-pass section, for the poles with the largest ω_0 , with $R_1 = R_2 = R_3 = R = 2 \text{ k}\Omega$.
- An SK high-pass section, for the poles with the smallest ω_0 , with $C_1 = C_2 = C = 10 \text{ nF}$ and $\mu = 1$.

a. Find the pole locations of the BP-filter using Matlab

```
OrderLPP = 2;
Om = [10 15]*pi*2e3;
[Numpoly DenomPoly] = butter(OrderLPP,Om,'s'); % Bandpass since Om
is a vector
Poles = roots(DenomPoly)
Poles =
    1.0e+004 *
    -1.2710 + 8.8077i
    -1.2710 - 8.8077i
    -0.9504 + 6.5862i
    -0.9504 - 6.5862i
```

b. Find ω_0 and Q for each of the two sections from the pole locations

```
omeg_0_biquad = abs(Poles)
Q_biquad = -2\abs(Poles)./real(Poles) % some function of Poles
omeg_0_biquad =
    1.0e+004 *
    8.8989
    8.8989
    6.6545
    6.6545
Q_biquad =
    3.5007
    3.5007
    3.5007
    3.5007
```

Section	$\omega_0 [10^4 \text{ rad/s}]$	Q
1 MFB-LP	8.90	3.5
2 SK-HP	6.65	3.5

c. Find the component values of the MFB-LP section

$$Q = \sqrt{\frac{C_1}{C_2}} \cdot \frac{1}{\frac{\sqrt{R_2 R_3}}{R_1} + \sqrt{\frac{R_3}{R_2}} + \sqrt{\frac{R_2}{R_3}}} = \frac{1}{3} \sqrt{\frac{C_1}{C_2}} \Rightarrow C_1 = 9Q^2 C_2$$

$$\omega_0 = \frac{1}{\sqrt{R_2 R_3 C_1 C_2}} = \frac{1}{3QR C_2} \Rightarrow \underline{\underline{C_2 = \frac{1}{3QR\omega_0} = 535 \text{ pF}}}$$

$$\underline{\underline{C_1 = 9Q^2 C_2 = 59.0 \text{ nF}}}$$

d. Find the component values of the SK-HP section.

$$Q = \frac{1}{\frac{\sqrt{R_1 R_2 C_1 C_2}}{R_2 C_2} + \frac{1}{R_2 C_1} + \frac{1-\mu}{R_1 C_1}} = \frac{1}{2} \sqrt{\frac{R_2}{R_1}} \Rightarrow R_2 = 4Q^2 R_1$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = \frac{1}{2QR_1 C} \Rightarrow \underline{\underline{R_1 = \frac{1}{2Q\omega_0 C} = 215 \Omega}}$$

$$\underline{\underline{R_2 = 4Q^2 R_1 = 10.5 \text{ k}\Omega}}$$

e. Option: Make a Spice-simulation to check the results

