

Signal Processing, lecture 1

Topics:

Introduction:

- Course overview
- Analog filters: Applications
- Ideal and real filters.

Filter design procedure and approximations:

- Normalization and de-normalization
- The Butterworth approximation

Literature:

The analog filter part of the course will be based on: Kendall Su: "Analog Filters", Kluwer Academic Publishers, 2nd ed. 2002, ISBN 1-4020-7033-0 (Springer: ISBN 978-1-4020-7033-4)

The book is available in electronic form at <http://www.en.aub.aau.dk> where you can read the book and print a few pages.

Topic	Pages ({*} ⇔ supplementary lit.)
Introduction, ideal filters, normalization and de-normalization	{1-2, 7-16} 3-7
Butterworth characteristics	25-30
Transfer functions	49-57

Supplementary: Lecture presentation "slides"

Exercises:

1.1

A Butterworth low-pass filter is wanted, with the two (standard) requirements:


- $20 \cdot \log |H(j \cdot 1 \text{ rad/s})| = -3 \text{ dB}$
 - $20 \cdot \log |H(j0)| = 0 \text{ dB}$
- Calculate and plot the pole locations for filters of order $n = 4$ and $n = 5$.
 - Find an expression for the transfer function from the pole locations for $n = 4$.
 - Check the results from a and b using Matlab

1.2

A 2nd order Butterworth low-pass filter is to be used in a class-D audio amplifier to pass the audio signal and attenuate the signal at the switching frequency.

- The attenuation at 20 kHz shall be 0.5 dB
 - The attenuation at the switching frequency shall be 30 dB
- For a normalized ($\omega_{3\text{dB}} = 1 \text{ rad/s}$) 2nd order Butterworth filter, find the radian frequency, where the attenuation is 0.5 dB.
 - For the normalized filter, find the radian frequency, where the attenuation is 30 dB, and find the transition band ratio, $\omega_{30\text{dB}}/\omega_{0.5\text{dB}}$.

- A 2nd order Butterworth filter with $\omega_{3dB} = 1$ rad/s, can be made using the circuit shown with $L_1 = 1.4142$ H and $C_2 = 0.7071$ F and $R_L = 1 \Omega$.
- c. Make a frequency scaling so that the scaled filter has an attenuation of 0.5 dB at 20 kHz. What is the needed frequency scaling factor?
- d. Find the frequency, where the scaled filter has an attenuation of 30 dB.
- e. Plot the magnitude of the transfer function (dB) in Matlab
- f. Make an impedance scaling to $R_L = 4 \Omega$ and find the new values, $L_{1,scaled}$ and $C_{2,scaled}$.

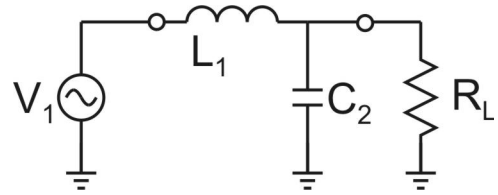

1.3

The following requirements are set for a Butterworth low-pass filter:

- The attenuation at ≥ 30 kHz shall be ≥ 20 dB
 - The attenuation at ≤ 10 kHz shall be ≤ 1 dB
- a. Find the necessary filter order.
 - b. Find the 3-dB bandwidth, when the attenuation at 10 kHz is chosen to be 1 dB.

Results:**1.1****1.2**

•

- a. 0.591 rad/s
- b. 5.62 rad/s , 9.51
- c. $6.65 \mu\text{H}$, $3.33 \mu\text{F}$, $212.6\text{e}3$
- d. 190 kHz
- e.
- f. $26.6 \mu\text{H}$, 831 nF

1.3

•

- a. 3
- b. 12.53 kHz