

2018-09-05/ MS/OKJ

Signal Processing, lecture 1

Suggested solutions to exercises:

1.1

A Butterworth low-pass filter is wanted, with the two (standard) requirements:

- $20 \cdot \log |H(j \cdot 1 \text{ rad/s})| = -3 \text{ dB}$


- $20 \cdot \log |H(j0)| = 0 \text{ dB}$

a. Calculate and plot the pole locations for filters of order $n = 4$ and $n = 5$.

$$p_k = e^{j\left(\frac{2k-1}{2n}\pi + \frac{\pi}{2}\right)} \quad k = 1, 2, 3, \dots, n$$

$$n = 4: \quad p_k = e^{j\left(\frac{2k-1}{8}\pi + \frac{\pi}{2}\right)} \quad \{k = 1, 2, 3, 4\} \quad \left\{ \begin{array}{l} e^{j\frac{5}{8}\pi} = -0.383 + j0.924 \\ e^{j\frac{7}{8}\pi} = -0.924 + j0.383 \\ e^{j\frac{9}{8}\pi} = -0.924 - j0.383 \\ e^{j\frac{11}{8}\pi} = -0.383 - j0.924 \end{array} \right.$$
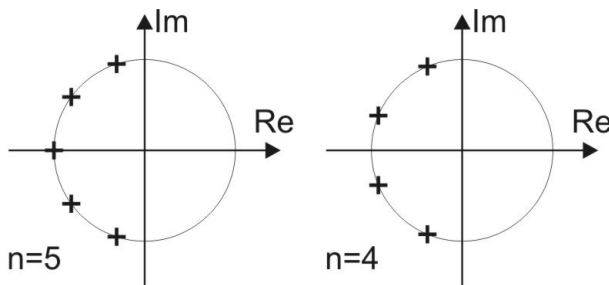
$$n = 5: \quad p_k = e^{j\left(\frac{2k-1}{10}\pi + \frac{\pi}{2}\right)} \quad \{k = 1, 2, 3, 4, 5\} \quad \left\{ \begin{array}{l} e^{j\frac{6}{10}\pi} = -0.309 + j0.951 \\ e^{j\frac{8}{10}\pi} = -0.809 + j0.588 \\ e^{j\frac{10}{10}\pi} = -1 \\ e^{j\frac{12}{10}\pi} = -0.809 - j0.588 \\ e^{j\frac{14}{10}\pi} = -0.309 - j0.951 \end{array} \right.$$



b. Find an expression for the transfer function from the pole locations for $n = 4$.

$$H(s) = \frac{1}{(s - e^{j\frac{5}{8}\pi})(s - e^{j\frac{11}{8}\pi})(s - e^{j\frac{7}{8}\pi})(s - e^{j\frac{9}{8}\pi})}$$

$$H(s) = \frac{1}{(s^2 + 2 \cdot 0.383s + 1)(s^2 + 2 \cdot 0.924s + 1)}$$

$$H(s) = \frac{1}{s^4 + 2.614s^3 + 3.416s^2 + 2.614s + 1}$$

c. Check the results from a and b using Matlab

`[dummy pole4 A0] = buttap(4);` % Returns the poles (and A0 = 1)

```

pole4
[dummy pole5 A0] = buttap(5);
pole5
denom_coeff4 = poly(pole4)           % Returns the a_n's
pole4 =
    -0.3827 + 0.9239i
    -0.3827 - 0.9239i
    -0.9239 + 0.3827i
    -0.9239 - 0.3827i
pole5 =
    -0.3090 + 0.9511i
    -0.3090 - 0.9511i
    -0.8090 + 0.5878i
    -0.8090 - 0.5878i
    -1.0000
denom_coeff4 =
    1.0000    2.6131    3.4142    2.6131    1.0000

```

1.2

A 2nd order Butterworth low-pass filter is to be used in a class-D audio amplifier to pass the audio signal and attenuate the signal at the switching frequency.

- The attenuation at 20 kHz shall be 0.5 dB
 - The attenuation at the switching frequency shall be 30 dB
- a. For a normalized ($\omega_{3dB} = 1$ rad/s) 2nd order Butterworth filter, find the radian frequency, where the attenuation is 0.5 dB.

$$|H_{norm}(j\omega_{0.5dB})|^2 = \frac{1}{1 + (\omega_{0.5dB})^{2n}} = 10^{-0.5/10}$$

$$(\omega_{0.5dB})^{2 \cdot 2} = 10^{0.5/10} - 1$$

$$\omega_{0.5dB} = \left(10^{0.5/10} - 1\right)^{1/4} = 0.591 \text{ rad/s}$$

- b. For the normalized filter, find the radian frequency, where the attenuation is 30 dB, and find the transition band ratio, $\omega_{30dB}/\omega_{0.5dB}$.

$$\omega_{30dB} = \left(10^{30/10} - 1\right)^{1/4} = 5.62 \text{ rad/s}$$

$$\omega_{30dB} / \omega_{0.5dB} = 9.51$$

- A 2nd order Butterworth filter with $\omega_{3dB} = 1$ rad/s, can be made using the circuit shown with $L_1 = 1.4142$ H and $C_2 = 0.7071$ F and $R_L = 1 \Omega$.

- c. Make a frequency scaling so that the scaled filter has an attenuation of 0.5 dB at 20 kHz. What is the needed frequency scaling factor?

$$\text{Freq. scaling factor, } k_f = (2\pi 20 \times 10^3) / 0.591 = 212.6 \times 10^3$$


$$L_1 = L_{1norm} / k_f = 6.65 \mu\text{H}$$

$$C_2 = C_{2norm} / k_f = 3.33 \mu\text{F}$$

- d. Find the frequency, where the scaled filter has an attenuation of 30 dB.

$$f_{30dB} = \omega_{30dBnorm} \cdot k_f / 2\pi = 190 \text{ kHz}$$

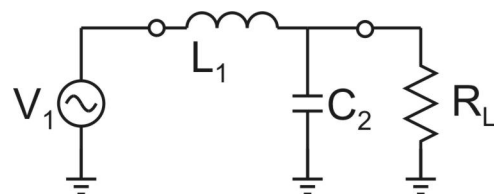
- e. Plot the magnitude of the transfer function (dB) in Matlab



```

n = 2; % Filter order
kf = 212.6e3; % Freq scaling factor
freq = logspace(3,6,1000); % Real frequency
om_norm = 2*pi*freq/kf; % Normalized radian frequency
HdB = -10*log10(1+om_norm.^(2*n));
semilogx(freq,HdB);
grid;
xlabel('Frequency [Hz]');
ylabel('Attenuation [dB]');
f_sw = freq(find(HdB+30<0,1,'first'))

```

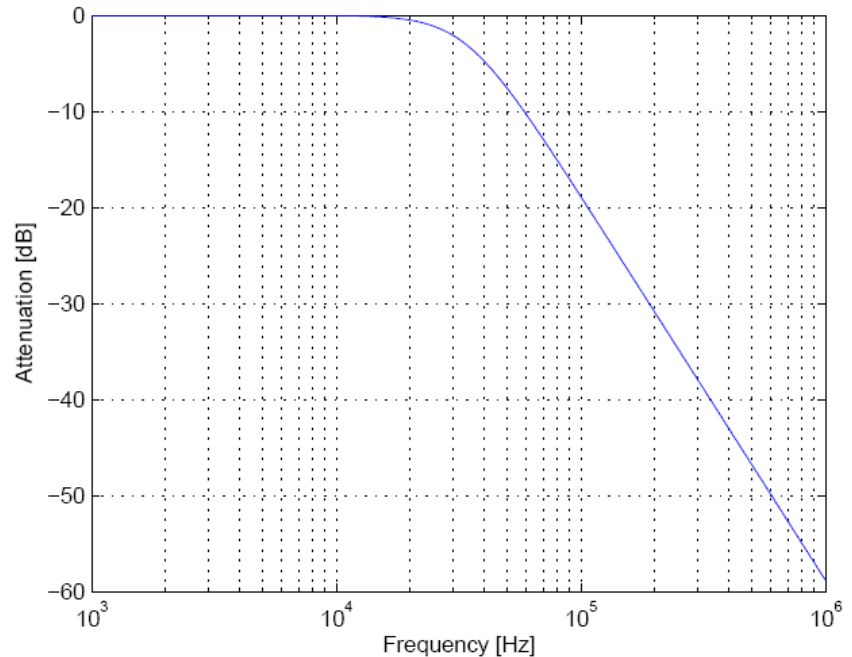

- f. Make an impedance scaling to $R_L = 4 \Omega$ and find the new values, $L_{1,scaled}$ and $C_{2,scaled}$.

Imp scaling factor, $k_z = 4/1 = 4$.

$$L_{1,scaled} = L_1 \cdot k_z = 26.6 \mu H$$

$$C_{2,scaled} = C_2/k_z = 831 nF$$

1.3

The following requirements are set for a Butterworth low-pass filter:

- The attenuation at ≥ 30 kHz shall be ≥ 20 dB
 - The attenuation at ≤ 10 kHz shall be ≤ 1 dB
- a. Find the necessary filter order
b. Find the 3-dB bandwidth, when the attenuation at 10 kHz is chosen to be 1 dB

$$n \geq \frac{1}{2 \log \frac{\omega_S}{\omega_P}} \log \frac{10^{\alpha_{S,dB}/10} - 1}{10^{\alpha_{P,dB}/10} - 1} = \frac{1}{2 \log \frac{30}{10}} \log \frac{10^2 - 1}{10^{0.1} - 1} = 2.7 \sim \underline{\underline{3}}$$

$$|H_{Norm}(j\omega)|^2 = \frac{1}{1 + \omega^{2n}} \sim -1 \text{ dB} \Leftrightarrow \omega_{1dB} = \sqrt[2.3]{10^{0.1} - 1} = 0.798$$

$$k_f = \frac{2\pi 10e3}{0.798} = 78702$$

$$f_{3dB,scaled} = \frac{k_f}{2\pi} 1 \text{ rad/s} = \underline{\underline{12.53 \text{ kHz}}}$$